 


2024年3月26日 19:14



- Zero value truth table

- Control truth table

[illegible]

- ALU control truth table
  - ALUOp1 and ALUOp2 are not used in this simulator because there are 5 possible operations: ADD SUB XOR OR and undefined. 2 bit cannot represent 5 possible operations.

Opcode	funct3	funct7	ALU Operation	ALU Control Signal
1100011	N/A	N/A	SUB (B-type for BEQ, BNE)	0110
0100011	N/A	N/A	ADD (S-type for SW)	0010
0110011	000	0100000	SUB (R-type)	0110
0110011	000	0000000	ADD (R-type)	0010
0110011	100	N/A	XOR (R-type)	0111
0110011	110	N/A	OR (R-type)	0001
0110011	111	N/A	AND (R-type)	0000
0010011	000	N/A	ADD (I-type)	0010
0010011	100	N/A	XOR (I-type)	0111
0010011	110	N/A	OR (I-type)	0001
0010011	111	N/A	AND (I-type)	0000
0000011	000	N/A	ADD (for LW)	0010
_ (default)	_	_	Undefined	1111

- ALU truth table

aluControl	Operation	Result	Zero Flag
0010	ADD	readData1 + readData2	"1" if result is 0, otherwise "0"
0110	SUB	readData1 - readData2	"1" if result is 0, otherwise "0"
0000	AND	readData1 & readData2	"1" if result is 0, otherwise "0"
0001	OR	readData1   readData2	"1" if result is 0, otherwise "0"
0111	XOR	readData1 ^ readData2	"1" if result is 0, otherwise "0"

#### Possible Improvement

- The most effective improvement is to change the single cycle behavior to a pipeline one. This improvement can utilize all non-active components, but should be aware of data hazard.